

Electrical Circuits

An electrical circuit consists of various element connected by wires. When the circuit is closed, electrical charges flow through the wire. Basic variables for measurement in circuits:

$Q(t)$: amount of charge in circuit

$I(t)$: current in circuit = flow of charge

These variables are related by the equation:

$$I = \frac{dQ}{dt}$$

To study circuits, we look at the change in electrical potential (the voltage) as you go around the circuit.

Elements of Circuits

1. **Resistor**: opposes current

E.g. light bulb

Potential difference (voltage drop) across a resistor is proportional to the current in the resistor:

$$V_R = RI \quad \text{Ohm's Law}$$

R is a constant of proportionality called the *resistance*.

2. **Inductor**: opposes change in current

Potential difference across an inductor is proportional to the rate of change of current:

$$V_L = L \frac{dI}{dt} \quad \text{Law of Induction}$$

L is a constant of proportionality called the *inductance*.

3. **Capacitor:** stores charge

Potential difference across a capacitor is proportional to the charge in the capacitor

$$V_C = \frac{Q}{C} \quad \text{Coulomb's Law}$$

C is a constant of proportionality called the *capacitance*.

4. The **source or applied voltage** is described by some known function of time, $V(t)$, which depends on the particular source.

E.g. battery or generator

Units

Q - coulomb

R - ohm

I - ampere

L - henry

E - volt

C - farad

The physical law governing electrical circuits is a statement of conservation of electrical potential energy.

Kirchhoff's Law The algebraic sum of the instantaneous potential differences around any closed circuit is zero.